

Simple sequencer experiment in LTspice -- ON: 1-2-3-4-5 / OFF: 5-4-3-2-1

D1-D5:
MBS1100 = as relay protection diode
or 1N4001, etc.

D6-15:
BZX84C6V2L = 6.2V Zener diode.


D16: silicon diode e.g. 1N4001.

R7-11:
representative 12VDC relay coil R.
for 120mA. Trim max. current higher
and equalize base currents by
adjusting R1-5 values.

R6+C1 sets time constant for fairly
linear voltage rise across C1 until
all relays operate. Result is fairly
similar delays from stage to stage.

Notes:

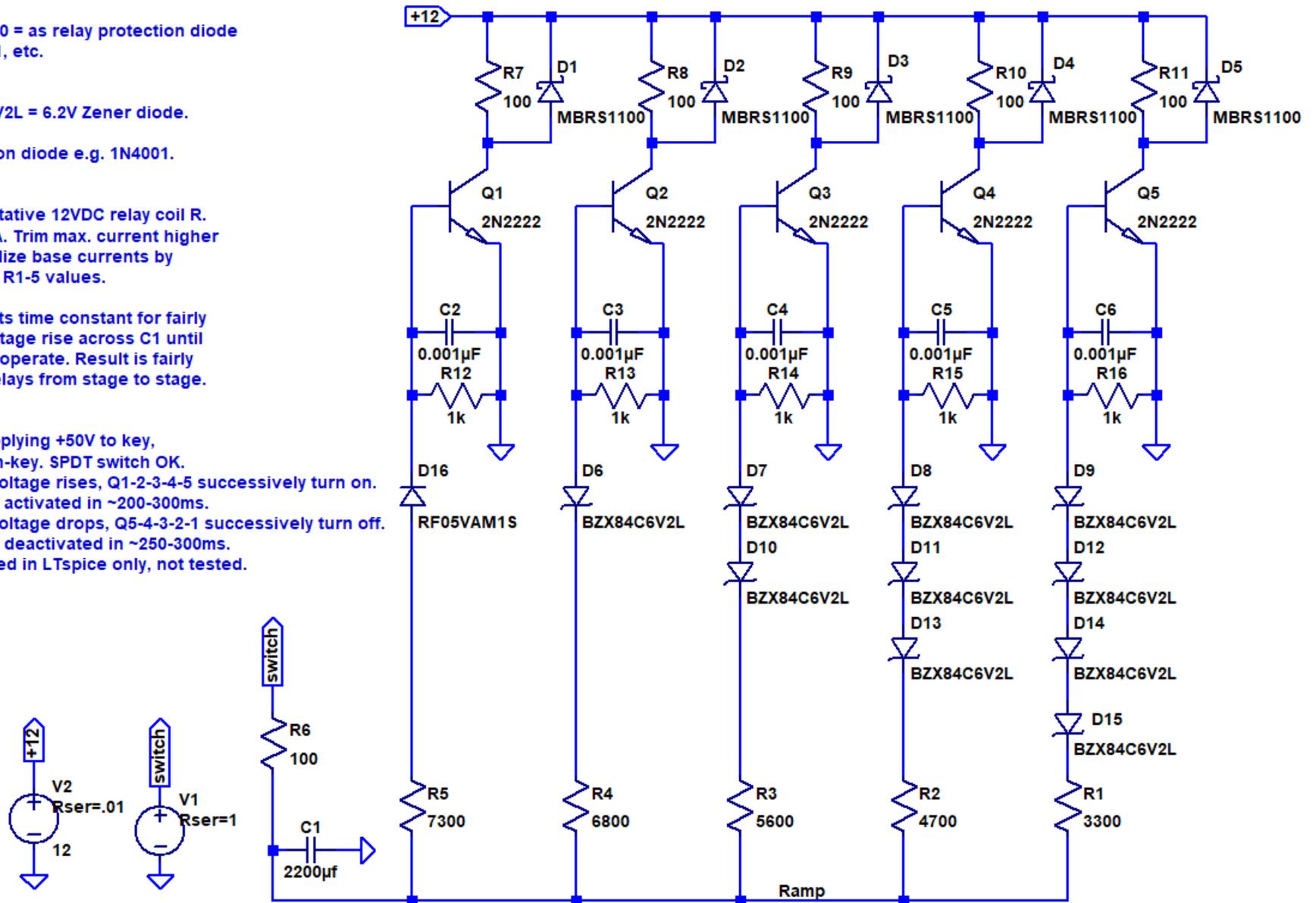- V1 is applying +50V to key,
- 0V to un-key. SPDT switch OK.
- As C1 voltage rises, Q1-2-3-4-5 successively turn on.
- all coils activated in ~200-300ms.
- As C1 voltage drops, Q5-4-3-2-1 successively turn off.
- all coils deactivated in ~250-300ms.
- simulated in LTspice only, not tested.



PWL(0 0 0.5 0 0.501 50 1 50 1.001 0 1.999 0 2 50 2.3 50 2.3001 0 3 0)

.tran 0 2 0

Patrick Jankowiak
BunkerofDOOM.com

