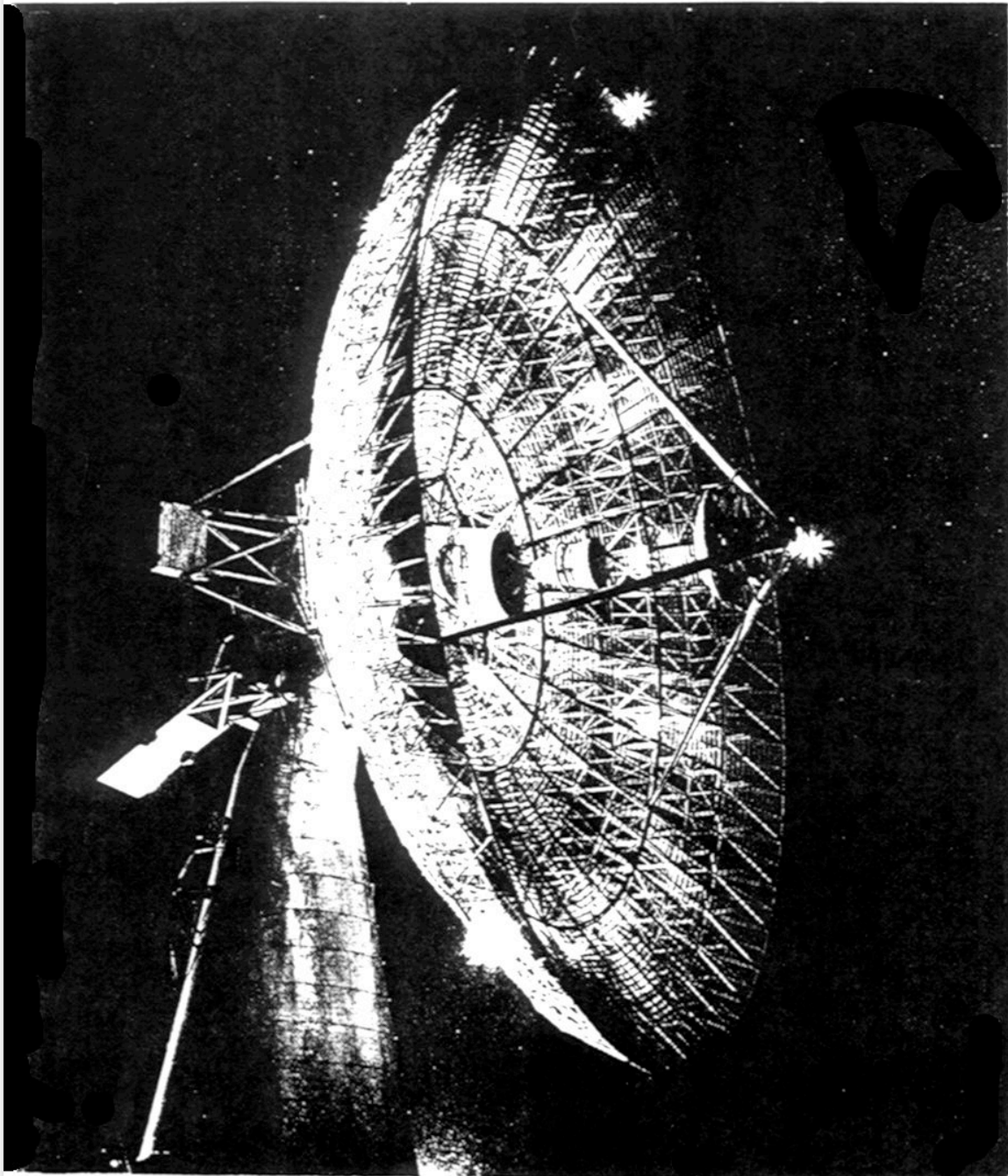


73

SEPTEMBER 1967

60¢

AMATEUR RADIO



73 Magazine

September 1967

Vol. XLVI No 9

Jim Fisk WIDTY
Editor

Kayla Bloom WØHJL
Assistant Editor

Jack Morgan KIRA
Advertising Manager

Published by
Wayne Green, W2NSD/1

ADVERTISING RATES

	1X	6X	12X
1 p	\$298	\$281	\$264
1/2 p	155	147	139
1/4 p	80	76	72
2"	42	40	38
1"	23	22	21

No extra charge for second color (red, usually) or bleed on full page ads. If you're interested in advertising to hams, get our full rate card and other information from Jack Morgan KIRA.

73 Magazine is published monthly by 73, Inc., Peterborough, N. H. 03458. The phone number is 603-924-3873. Subscription rate: \$5.00 for one year, \$9.00 for two years and \$12.00 for three years. Second class postage paid at Peterborough, New Hampshire and at additional mailing offices. Printed in Pontiac, Illinois, U.S.A. Entire contents copyright 1967 by 73, Inc. Postmasters, please send form 3579 to 73 Magazine, Peterborough, New Hampshire 03458.

SEPTEMBER 1967

The Synchronous Detection Process	W3DUQ	6
If you must use AM, get the most out of it.		
A 160-Meter Sidewinder	W6JTT	12
A sideband package for the low band.		
Building Blocks	WB2EGZ	17
A 12 to 18 MHz receiver for VHF converters.		
VSWR Supreme	W4BRS	20
A compact VSWR unit that can be built into your rig.		
Dual-Band Use of Single-Band Beams	W2EEY	26
Get the most use out of those antennas.		
Grounded-Grid Filament Chokes	W6RET	30
How to design and wind your own.		
200 Hertz CW Filter	K7UDL	34
Maximum selectivity with telephone coils.		
Observations of Note by a VHF Addict	WB6JLC	37
Hilltopping in Southern California.		
Getting a Start in Amateur Television	WA2EMC	40
Off on the right foot.		
A Compact Linear Amplifier	VE2AES	44
500 watts in a small package.		
Cathode Keying Filter	W6BLZ	48
Getting rid of key clicks.		
A Simple Resistance Bridge	VE3AHU	51
Precision resistance measurement at low cost.		
Compact Heat Sinks	Ives	52
Using copper pipe caps for cooling semiconductors.		
Evaluating Antenna Feed Systems	W7QAG	56
Using time domain reflectometry.		
Cheapskate's "On the Air" Sign	WN3EWV	62
Eliminating in-shack interference.		
Relay Energization in Fixed and Mobile Equipment	VE4RE	64
Just what the title says.		
How to be a Ham—By Really Trying	VE3GLX	66
It isn't hard if you try.		
Do-It Yourself Mobile Mount	W6APE	68
Nice looking but simple floor mount.		
Washing Out Your (Antenna) Shorts	W3RZD	70
Keep road salt and water out of your mobile antenna.		
A Polarity Sensitive Meter for the Sightless	WA2BCX	72
Used for checking diodes, capacitors and resistors.		
Climbing the Novice Ladder: Part X	W7OE	74
FN offers Judy and Joe some sage advice.		
Trindade Island DXpedition	PY2BZD	82
The DX-capades of PY2BZD/PYØ.		
Gus: Part 27	W4BPD	84
Gough Island.		
DX'ing	W2NSD/1	88
How to get the most out of chasing DX.		
The Knight-Kit KG-663 Low-Voltage Power Supply	WIDTY	94
An excellent power supply for the ham shack.		
Heathkit SB630 Control Console	W2DJL	96
Handsome mate to the SB301 and SB401.		

The View from Here	2	Antenna Coil Protection	71
W2NSD/1	4	Sharpening Chassis Punches	71
DL4IO-3690	32	WTW News	80
Increased Twoer Selectivity	49	Propagation	92
Simple Test Leads	54	New Books	106
Mobile Installations	63	Letters	113
Tuning RTTY with a Piano	69	Caveat Emptor	123
Ad Index		128	

The Synchronous Detection Process

If you want to get the most out of AM or DSB communications, try the synchronous detector. With a synchronous detector at both ends of an AM communications link, the system is as effective as single sideband.

Synchronous detection, when adapted to a communications receiver with an *if* band-pass of six kHz or better, provides an excellent means of single signal reception, along with the capabilities of almost complete rejection of non-synchronous components such as single sideband, RTTY, unmodulated carriers, static, and most spurious sideband splatter emanating from off-frequency signals. It provides a means of phase locking the detector on synchronous type transmissions such as DSB with carrier, DSB without carrier, NBFM, and phase modulation.

A block diagram, shown in Fig. 1, gives the basic elements of the system used at W3DUQ. Blocks marked with an X are the ones necessary for basic synchronous detection if the stereo synthesizer, as will be described later, is not desired. The basic sys-

tem utilizes eleven dual purpose tubes.

Following the block diagram, the signal input is applied to each 7360 demodulator (V1, V2), and the local 455 kHz oscillator voltages are applied to each demodulator in phase quadrature (90° apart). Assume, momentarily, that the "I" channel local oscillator injection voltage is the same phase as the carrier (transmitted or suppressed) component of the AM signal. Then the in-phase or "I" channel will contain the demodulated signal, while the "Q" channel will contain no audio, as its injected local oscillator voltage is shifted 90°. Now, if the local oscillator or signal drifts slightly, the "I" channel will be unaffected, but the "Q" channel will produce some audio. This will have the same polarity as the "I" channel audio for one direction of local oscillator or signal drift, and opposite polarity for the opposite direction of local oscillator or signal drift. The "Q" channel level will be proportional to the oscillator drift, for shifts of 300 Hz or less. By simply combining the "I" and "Q" audio in an audio phase discriminator (V4 and associated circuitry), a dc control signal is obtained. This control voltage tunes the oscillator (V5B) via the reactance tube (V5A), and returns or locks the oscillator to the correct phase where audio is present only in the



The synchronous detector.

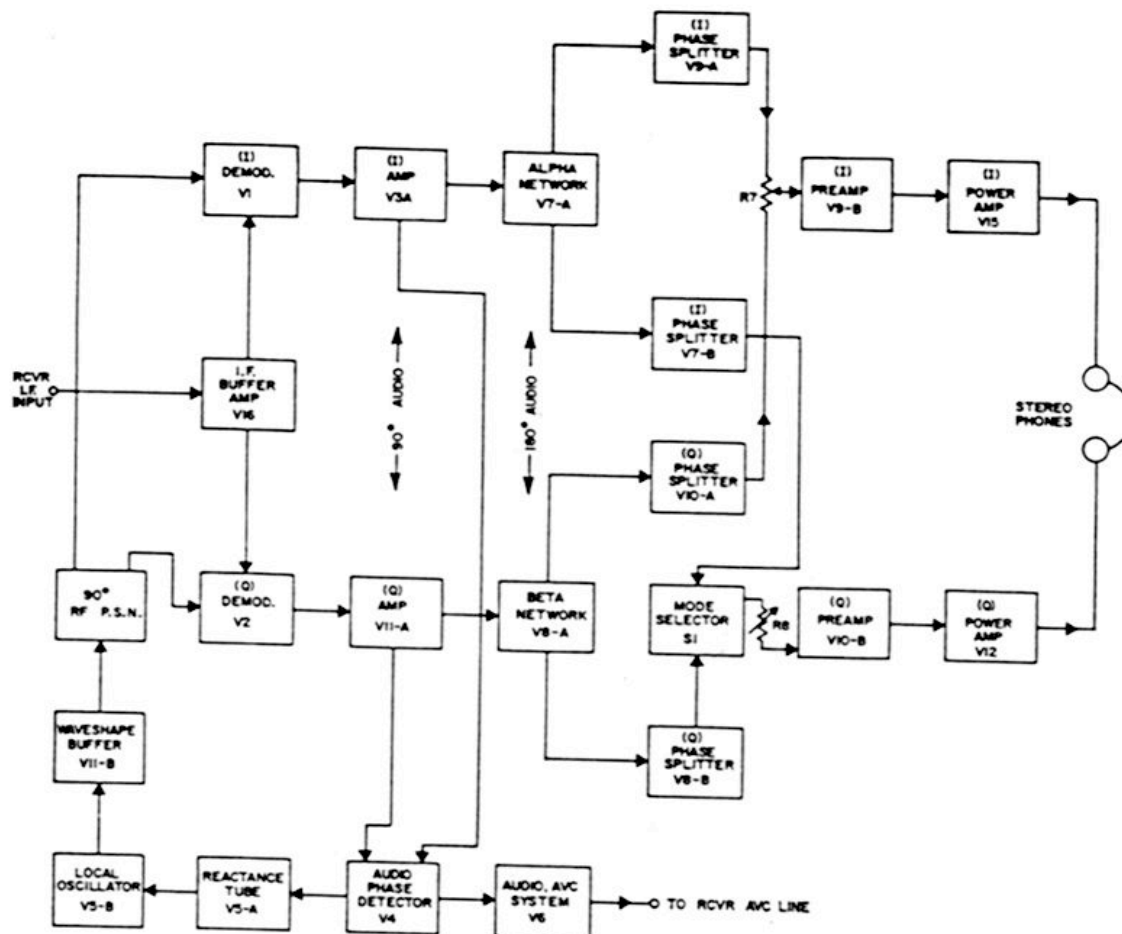


Fig. 1 Block diagram of the synchronous detector

"I" channel.


The audio phase detector delivers a dc voltage only when the "I" and "Q" signals have in-phase (synchronous) components. Since the "I" and "Q" audio will be in phase quadrature in any case, where the like sidebands do not exist on each side of the carrier, the phase detector provides no AFC voltage for SSB, static, or CW signals, and is therefore totally unaffected by this type of interference.

If the "I" and "Q" audio outputs are taken through *alpha* and *beta* networks respectively (90° audio phase-shift networks), interference rejection on the order of 60 dB may also be obtained. When locked on a signal containing interference on the lower sideband, for example, the "I" channel produces audio resulting from both locked signal sidebands plus lower sideband interference, while the "Q" channel contains only the interfering audio on the lower sideband. Phase cancellation, by combining the two

audio outputs from the *alpha* and *beta* networks, will remove the interference while still adding the desired information contained in both sidebands. By simply reversing the take-off points from the *alpha* and *beta* network outputs, similar rejection is obtained for interference contained in the upper sideband.

With the addition of the stereo synthesizer circuits, one output channel will contain the synchronous signal plus interference contained in the lower sideband, while the other channel contains the synchronous signal plus interference contained in the upper sideband. By phase cancellation, the brain (being the ultimate computer), picks out the synchronous signal while rejecting the undesired interference contained in *both* of the sidebands, and all you hear, basically, is the synchronous signal you *want* to hear!

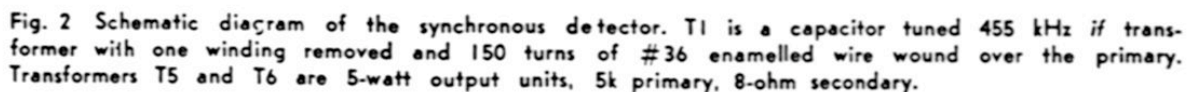Similarly, by unlocking the dc correction signal, SSB signals may be received in much the same manner of the good old standby—



demodulators are placed in a minimum ac field, or hum in the system will result, due to the high sensitivity of these beam deflection tubes.

Standard wiring procedure should be followed, with leads as short as possible, and

Care *must* be taken to ensure that the 7360

DC Voltages—Synchronous Detector Without *if* Signal

Tube No.	Type	1	2	3	4	5	6	7	8	9
V1	7360	5	150		Fil	Fil	80-100	80-100	25	25
V2	7360	5	150		Fil	Fil	80-100	80-100	25	25
V3	12AU7A	75		3.5	Fil	Fil				Fil
V4	12AU7A	240		11	Fil	Fil	240		11	Fil
V5	6AN8	60	—1	4.7	Fil	Fil	200	100		3
V6	12AU7A	247		8	Fil	Fil		0-50	0-12	Fil
V7	12AT7	240	5.5	8	Fil	Fil	212	6.5	10	Fil
V8	12AT7	240	5.5	8	Fil	Fil	212	6.5	10	Fil
V9	12AT7	212	6.5	10	Fil	Fil	120		1.7	Fil
V10	12AT7	212	6.5	10	Fil	Fil	120		1.7	Fil
V11	12AU7A	75		3.5	Fil	Fil	246		2.5	Fil
V12	6AQ5A		15	Fil	Fil	246	250			
V13	OB2	250	150		150	250		150		
V14	OA2	150				150				
V15	6AQ5A		15	Fil	Fil	246	250			
V16	12AX7	240		3.2						

Notes: Oscillator injection at V1, V2 is 6V p-p; maximum signal at V4 grids to be set at 8V p-p with R1; audio at V9b, V10b grids 100 mV p-p; adjust R2 for —1 volt dc on oscillator grid; set AVC depth control for 8-10 volts p-p at V4 grids with external BFO on and detuned 1 kHz.

the oscillator-reactance tube and associated circuitry should be kept away from the rest of the circuit as much as possible, to avoid 455 kHz pick-up by audio circuits.

Receiver modification and avc set-up

Take *if* out of the receiver (455 kHz) at the plate of the last *if* amplifier stage, through a 20 pF capacitor to RG62/U coaxial cable, to the grid of V16.

Modify the receiver avc switch to provide an external input position for the detector audio hang AVC voltage. Peak the *if* transformer in the plate of V16 with the rf gain wide open, the AVC switch in *external* receiver AVC, the receiver bfo or crystal calibrator on, and the detector oscillator detuned one kHz from the center of the *if* passband. Note the S-meter reading. Now switch the receiver to *internal* AVC, and note the S-meter reading. If the two meter readings are more than 5 dB apart, adjust the value of R1 (33k) until the meter readings agree.

Quadrature set-up

Tune the local oscillator to the center of the receiver *if* passband (you can use the receiver bfo for this), and set-up the oscillator injection quadrature, and alpha-beta networks as follows.

With the receiver tuned 1 kHz from an unmodulated carrier, set switch S1 to the position giving the least audio output, and alternately adjust the 8-50 pF trimmer in the oscillator quadrature circuit, and R8 for minimum audio output at "Q" preamp output. Now adjust R7 for minimum audio output on its rejected sideband at "I" preamp

output.

If the 8-50 pF trimmer adjustment is not the same for the opposite sideband selection on S1 (retune receiver to 1 kHz on the other side of zero beat for this test), the alpha and beta networks are off balance and can be brought in by judiciously trimming the 7k and 2k plate and cathode resistors on V7a and V8a, while adjusting the 8-50 pF trimmer and R8 until a minimum audio output results on either sideband.

Audio phase discriminator set-up

1. Short R3 to ground.
2. Tune the receiver 1 kHz from an unmodulated carrier (crystal calibrator works fine here) and adjust the rf gain for four volts rms audio on the plates of V3a and V11a.
3. Connect a dc VTVM or dc oscilloscope to TP1 and adjust R4 for minimum dc.
4. Move the VTVM to TP2 and adjust R5 for minimum dc.
5. Move the VTVM to TP3 and adjust R9 for minimum ac.
6. Remove ground from R3 and adjust R6 for minimum ac at TP3.
7. Repeat steps 3 and 4 until step 6 yields no ac output.

Notes

1. The output at the preamp output jacks is approximately 200 millivolts peak to peak.
2. For stereo reception, adjust the two 500k volume controls and the speaker phasing switch (using stereo headphones), until minimum interference on a locked synchronous signal is observed.

3. Adjust the compression depth control (500k) along with R1 for best synchronous locking. Value should come out on the depth control to about 400k.

4. S1 positions, starting at full counter clockwise:

- a. Reject upper sideband.
- b. Reject lower sideband.
- c. Stereo (reject lower "Q", reject upper "I" on earphones).
- d. Receive lower sideband-AFC off.
- e. Receive upper sideband-AFC off.

5. For best synchronous locking on double sideband signals, the receiver should be tuned 100 Hertz or closer to signal zero beat.

6. Set VR current (V13, V14) for 2.2 volts dc across the 100-ohm resistor at V13 pin 1 using the 2.5k, 25-watt adjustable resistor.

7. Set plate voltage for V12, V15 (6AQ5's) for 270 volts, using the 3k, 25-watt adjustable resistor.

8. If the stereo feature is not desired, eliminate V9, V10, V12, V15, and take the audio output from the center tap of R8.

Now sit back and enjoy QRM free reception.

In 1965, a test involving over two hundred students was conducted at Cambridge University, in England. Under controlled conditions, two transmitters were put on the air; one AM, the other SSB. The SSB transmitter was running twice the power output of the AM transmitter. Two identical receivers were set-up, one with a product detector for SSB reception, the other with a synchronous detector for AM reception. Each student was to copy a message, first from one receiver, then the other.

Then white noise was injected into both receivers, 3 dB at a time. In the end, the AM signal, running one-half the power output, was easily copied with over 6 dB more white noise injected into the receiver, while the SSB signal was completely washed out. So you see, it's not the mode of transmission so much as it is the method of detection.

Let's get rid of those outdated, wideband, distorted telephone quality single sideband gizmotchies; and put some good, narrow, maximum intelligibility advanced modulation back on so we may soon rid the bands of 30 kHz wide signals and once again enjoy *good, solid* communications.

. . . W3DUQ

