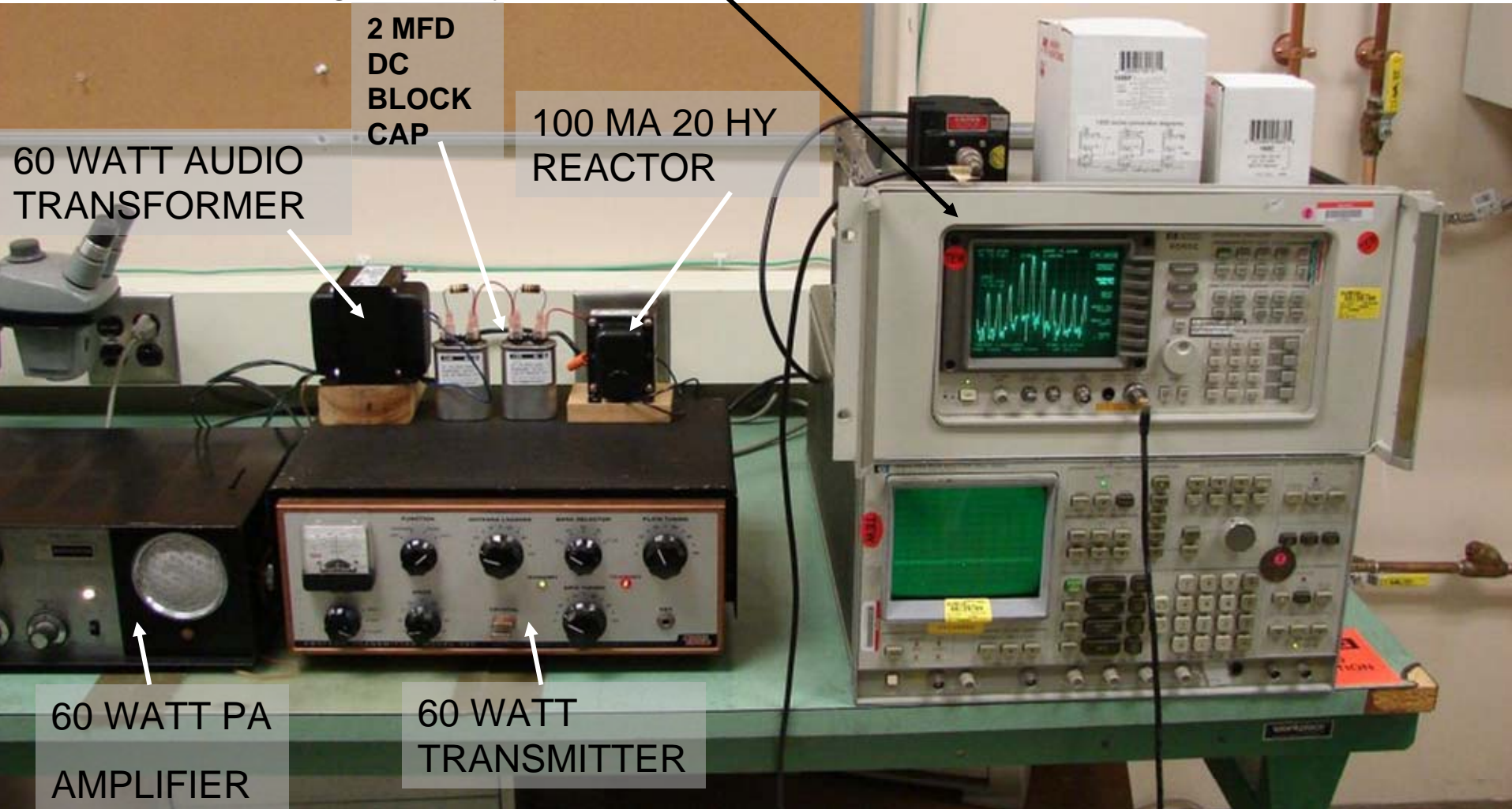
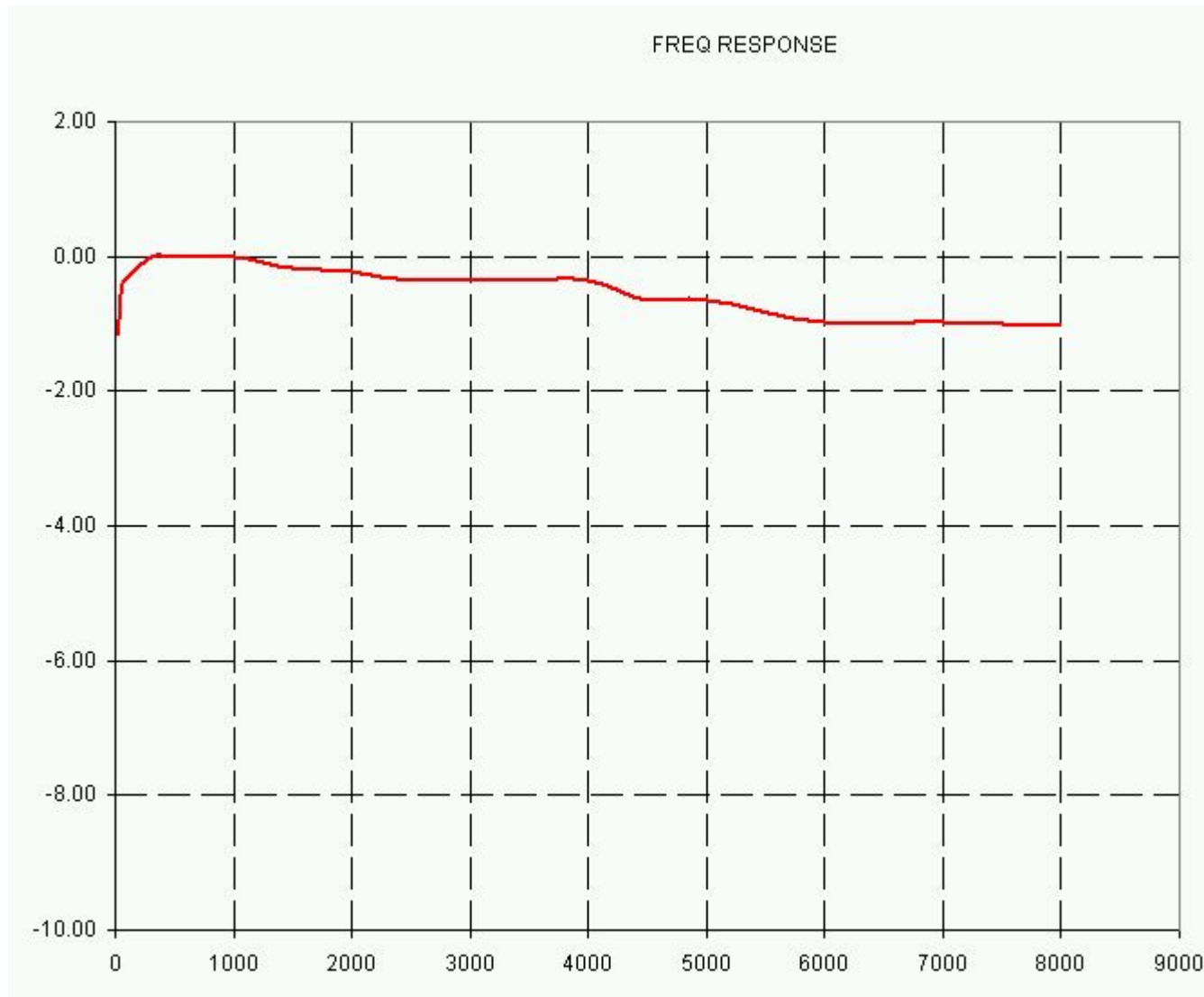


- Modified Heising AM modulator. A 60 watt pro-grade PA amp is used in conjunction with an audio transformer connected 16 ohm to 16 ohm. What was the primary is now the secondary @ 5000 ohm Z.
- Two 4 mfd caps are connected in series to form a 2 mfd blocking cap.
- The 20 hy choke is used as a Heising reactor. The resultant AM spectrum is shown indicating relatively low THD.



EICO 720 Frequency Response (dB)



EICO 720 THD TEST

