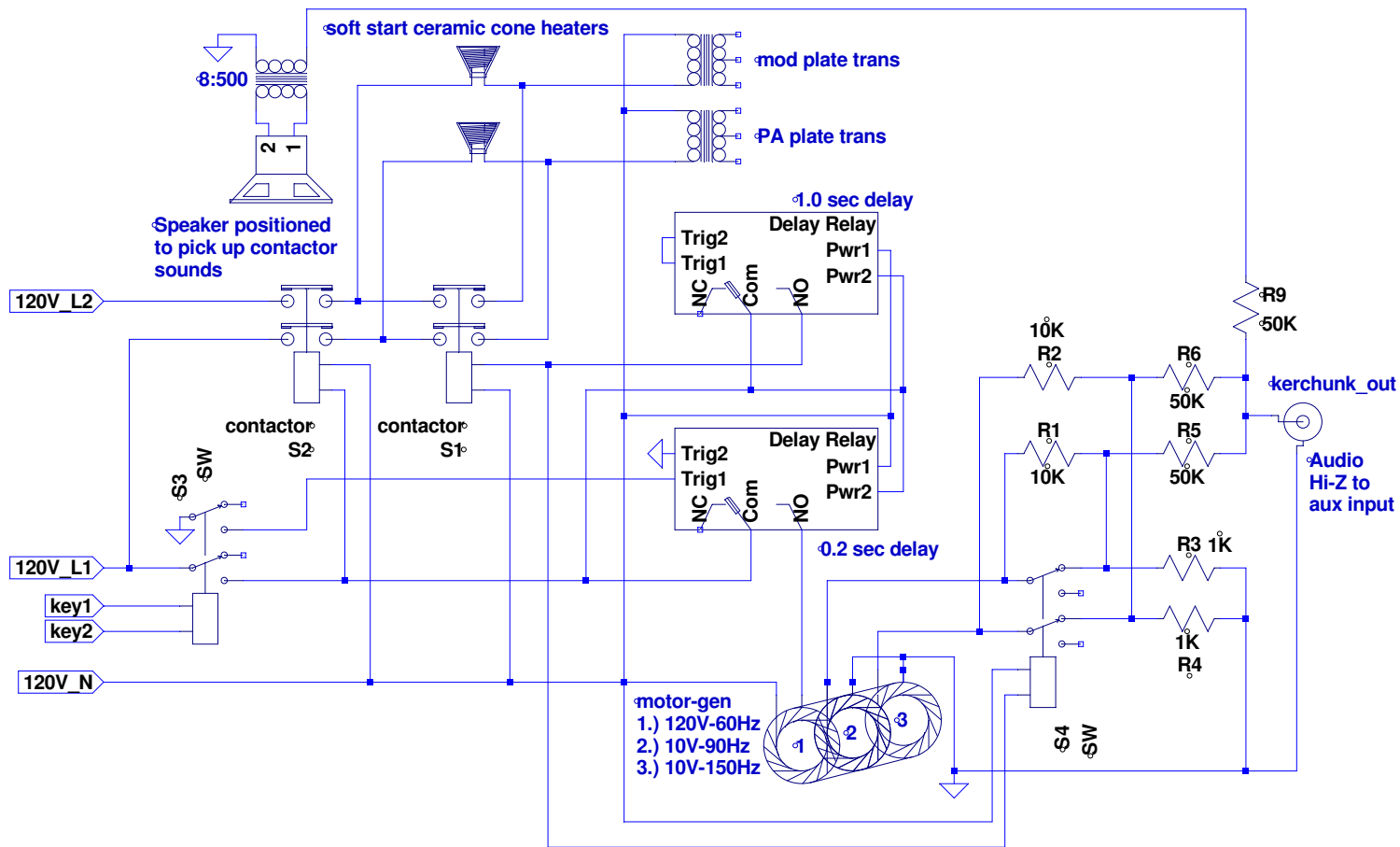


"Kerchunk Simulator" with Radio Moscow "dirty filter" 150HZ sound!



Sequence:

120V applied when TX is on

Key1-Key2 applied

contactor S2 engages starting soft-start and transmitting "low power" and speaker picks up echo of S2 and Delay 1 starts for 0.2 seconds

carrier comes up to about 1/3

after 0.2 seconds: MG winds up making "Radio Moscow" sound

After 1 second: contactor S1 engages and TX goes to full power and speaker picks up sound of S1 and MG set audio attenuated by 10dB and TX is used for speech

Key1-Key2 removed

power removed from all timers and relays system is reset