

Article Update for Viking II – CDC

Speech Amplifier and Modulator:

ER #324 (May/2016) discussed some suggested upgrades to the Viking II – CDC model. In that article, the Hammond 124E and 124D interstage transformers were mentioned as replacements for the original interstage transformer. Only the Hammond 124E circuit was given. If one uses the 124D, appropriate changes to the circuitry will have to be made since this transformer has a 1.54:1 turns ratio, whereas the Hammond 124E has a turns ratio of 3:1. **Further testing shows the Hammond 124D to be preferable because of its increased driving ability and lower crossover distortion.**

The speech amplifier and the modulator schematics, Figures 1 and 2, reflect those changes needed for the Hammond 124D.

Modulator Screen Voltage Regulator:


Figure 3 shows a 300V screen regulator for the modulator tubes to further reduce distortion in the audio chain. This regulator is based on a FET as the active device.

One other Note: In order to reduce stray RF in the bias circuit, a 0.001 uF ceramic disk of 1kV at the Final's grid circuit is needed. The preferable location for this capacitor is at the choke's bias supply side just above the grid choke, with the other lead of the capacitor to the Final's ground bus immediately to the right of the choke.


Voltages marked with a "*" are Keydown in AM or "Phone" mode under the following conditions:

Frequency = 3.880 MHz,
VFO 122 attached,
Final Grid Current = 5 mA,
Final Plate Current = 280 mA,
Final Screen Voltage = 297V,
Resting Modulator current = 55 mA.
HV = 700V,
AC input voltage = 120V,
Resting Carrier = 110 Watts.


Viking II - Speech Amp and Driver

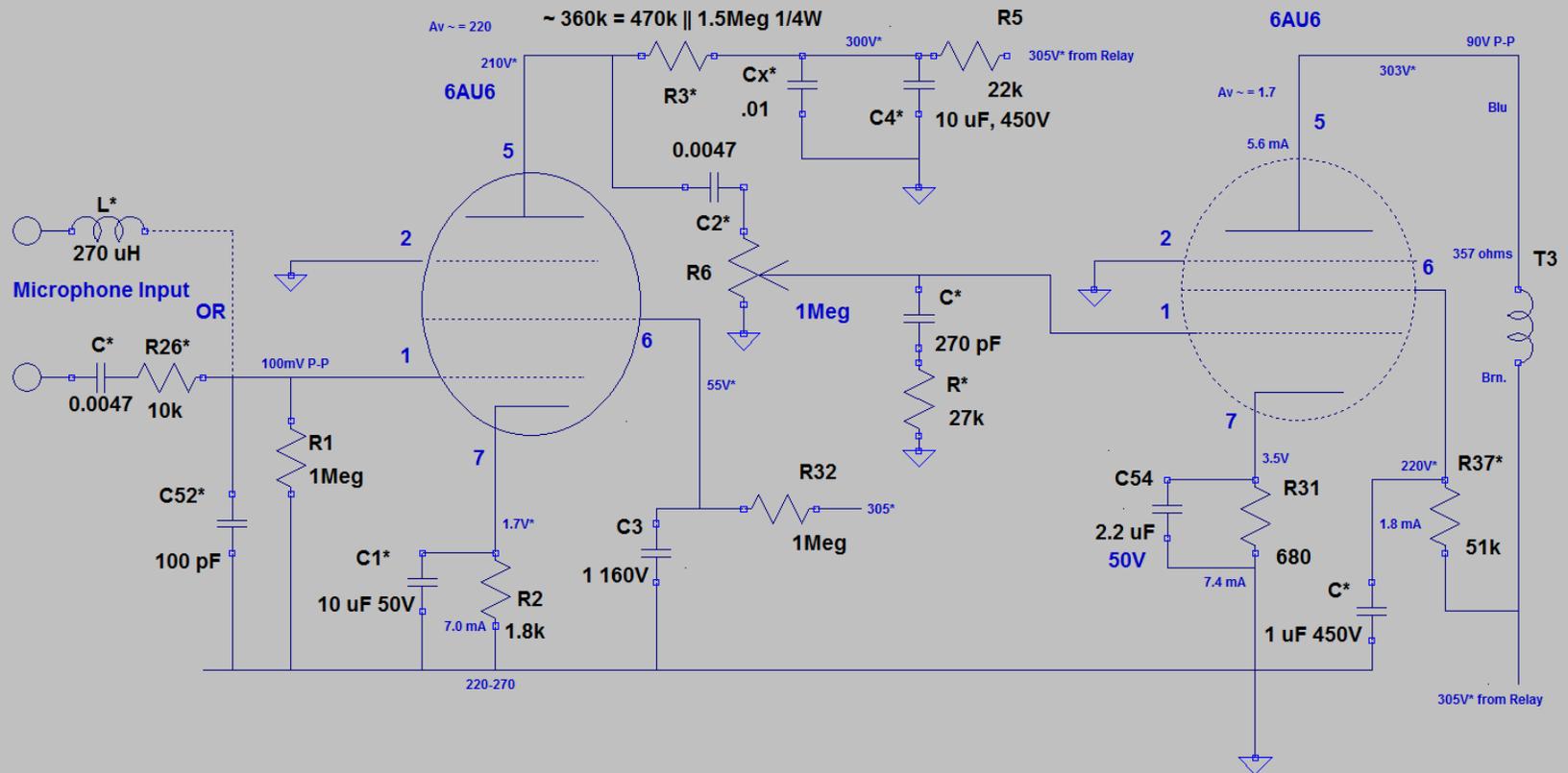

Viking II - Modulator

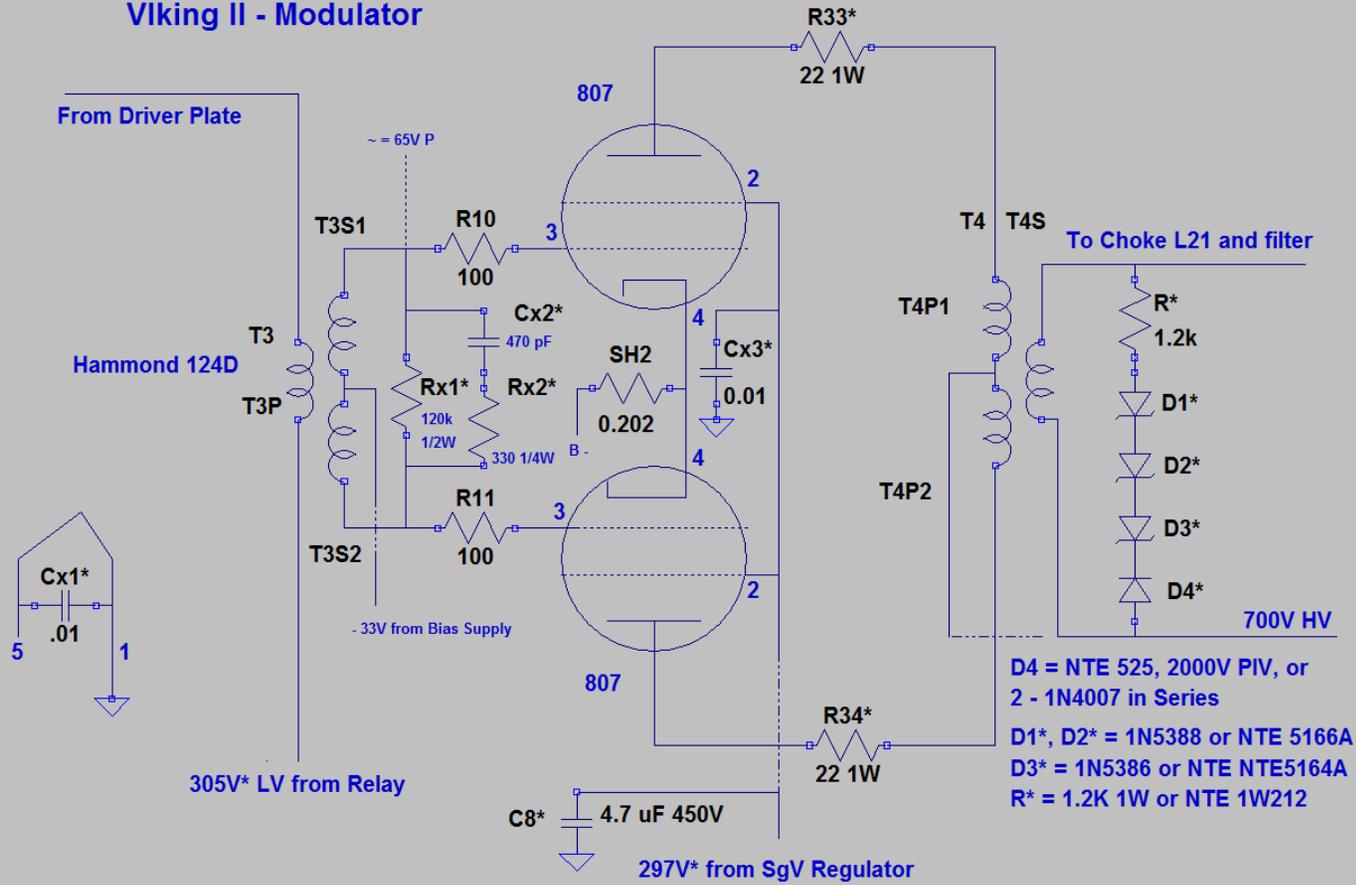


Viking II-CDC Bias Supply

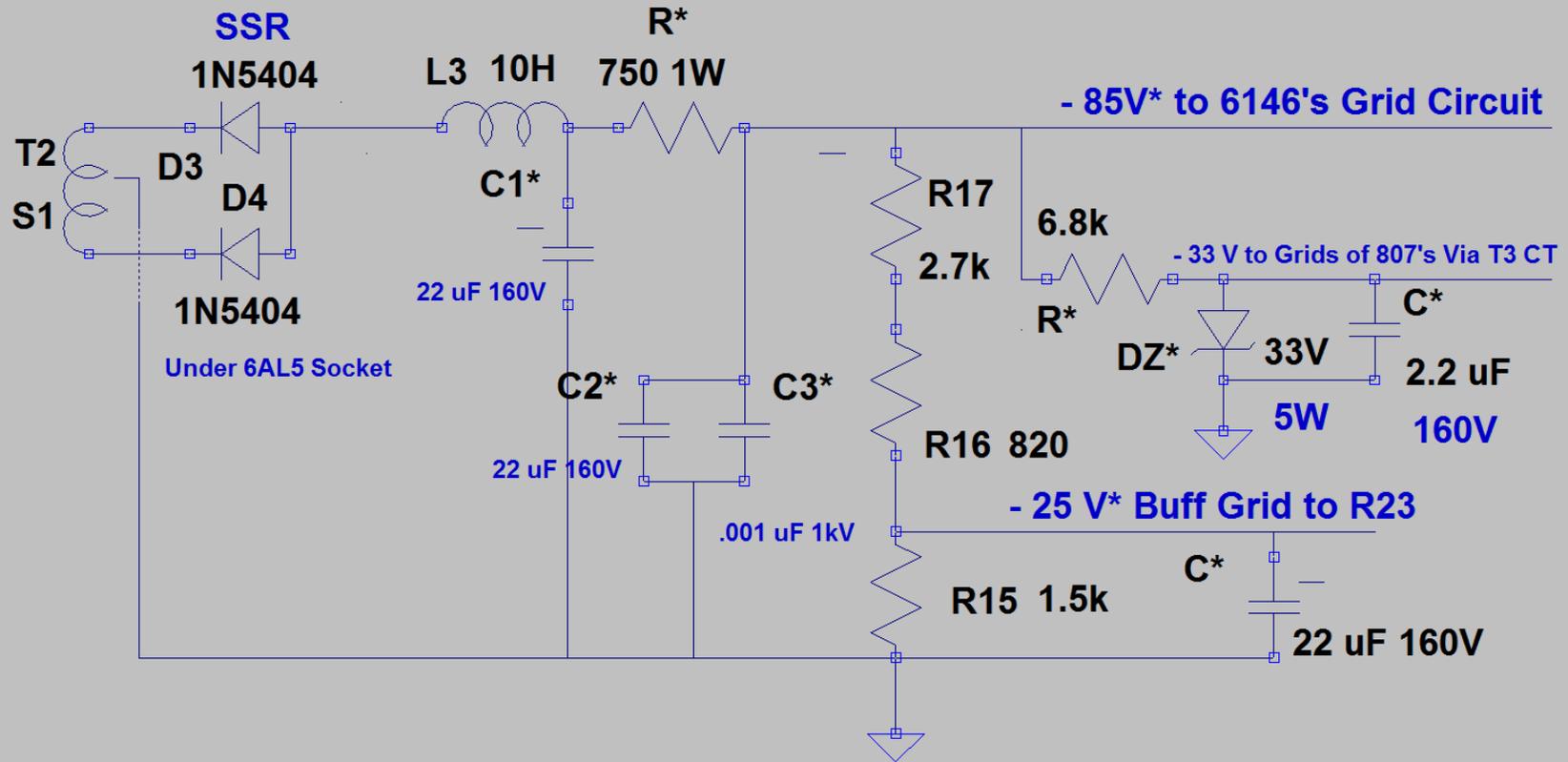

Viking II - RF Final Filter Circuit

Improves Audio Bandwidth

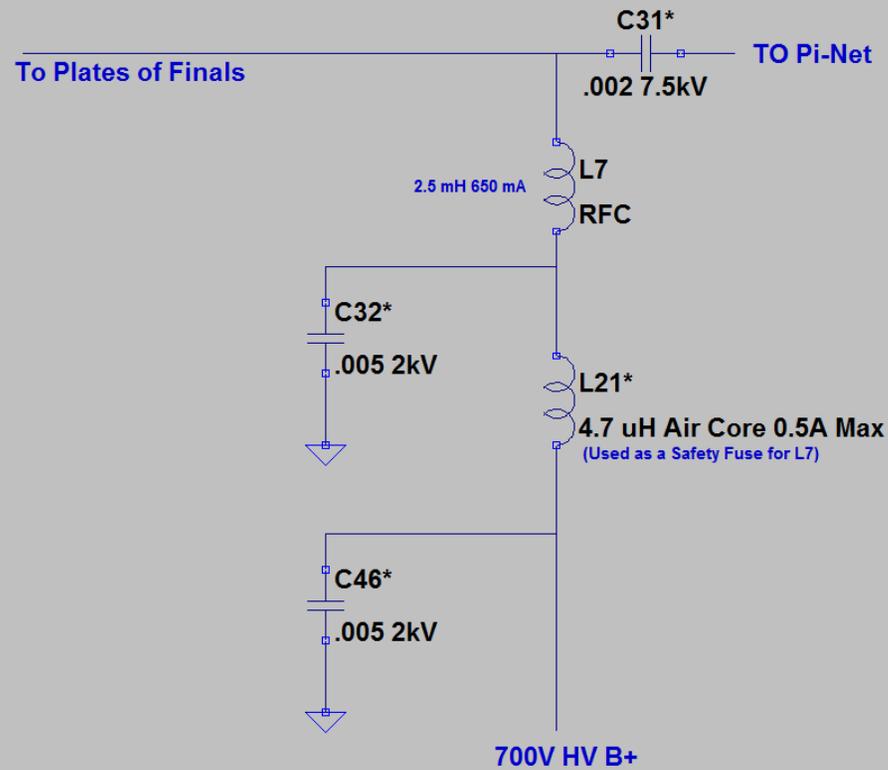

Viking II Clamp Circuit

6AQ5A/6005/6HG5

