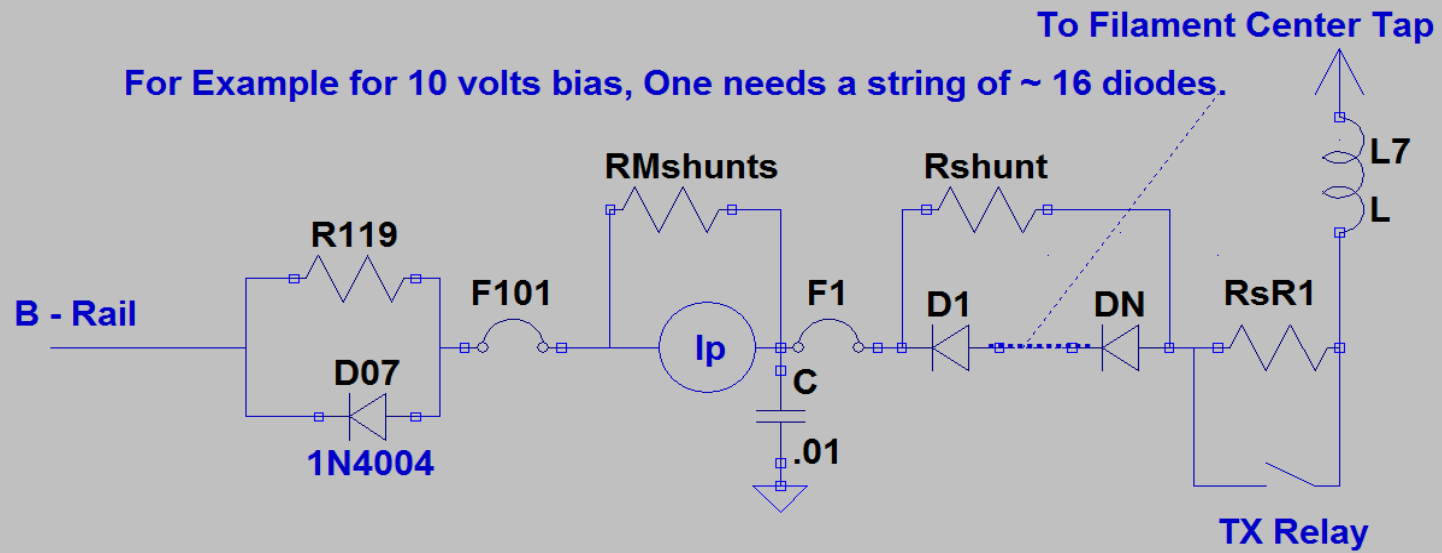


Biassing for 3-500Z's with a Diode String

For Example for 10 volts bias, One needs a string of ~ 16 diodes.



Biasing for 3-500Z's with a Zener

