
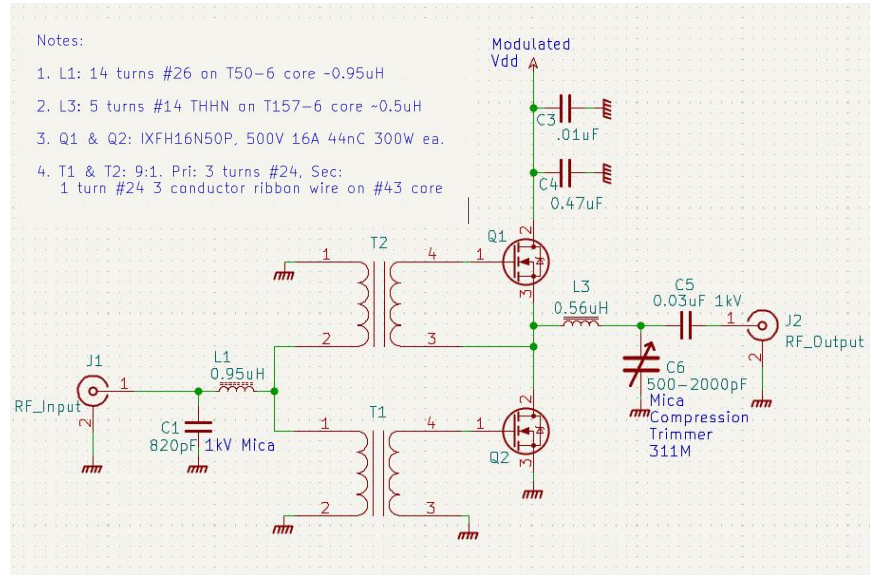

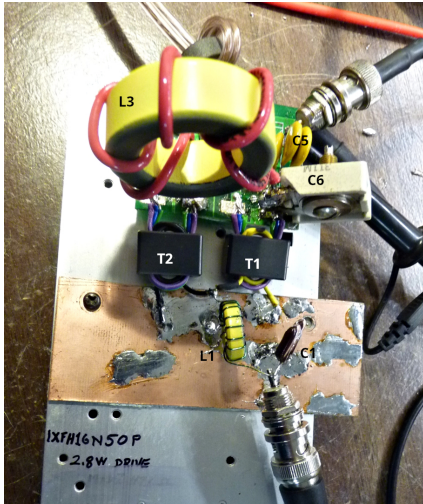
# A Half-Bridge Class D PA for 40 meters


WO1U Mike 3-8-2024

Here is a transformer driven Class D half-bridge amplifier. It can hit >80% efficiency. The fact that a Voltage Mode Class D amp can work efficiently on 40 meters is a testament to why I continue to use the IXFH16N50P mosfets. The PC board shown is chopped up from a full-bridge board I did >10 years ago.


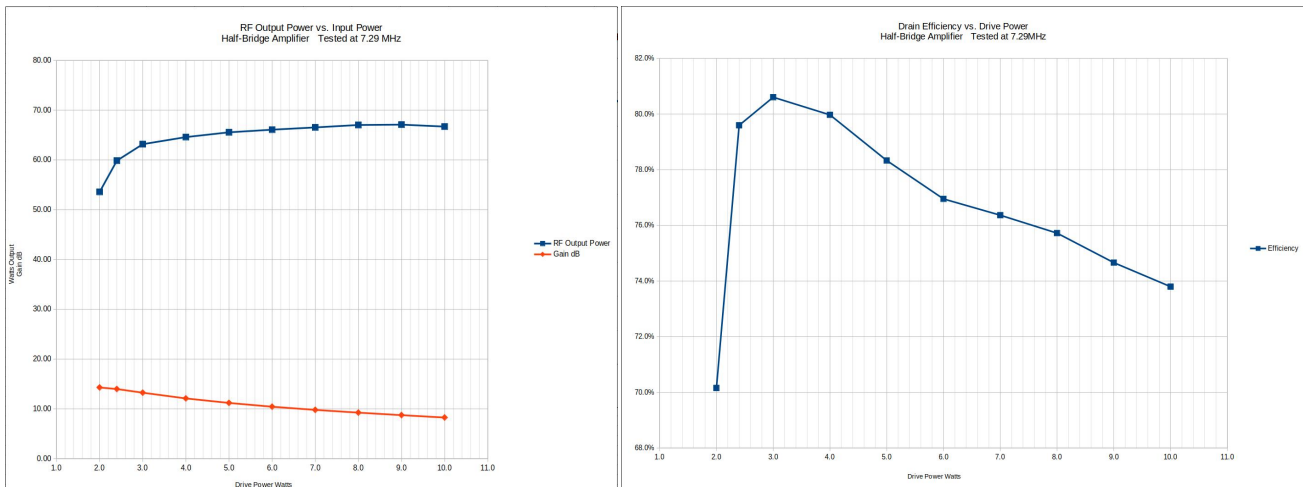
## Test Data:

Test Conditions, except as noted otherwise: Vdd = 60.2V, F = 7.29MHz, Load = 50 ohms, Input VSWR = 1.1:1



Note the gate-side secondary winding of the input transformers is 3 conductors 24 AWG ribbon cable. Lowest practical DC resistance and / or inductive reactance is needed in the gate circuits. Brass tube and ferrite sleeve type transformers, such as the CCI RF-400 is preferred for that reason, but in absence of those, the above transformer design is as close to the same performance as RF-400s (9:1 #43) as I have been able to hand-make. Cores are Fair-Rite part number 2843010402.

# A Half-Bridge Class D PA for 40 meters

WO1U Mike 3-8-2024

## Output Spectrum:

On a scope, the waveform looks reasonably sinusoidal. Spurs and harmonics are surprisingly manageable for a saturated switching amplifier. Adding a 5 element LPF reduces all spurs and harmonics to better than -50dBc.

(LPF = Series 2.3uH, 470pF to ground, series 3.2uH, 470pF to ground, series 2.3uH provides 7.4MHz cutoff.)

